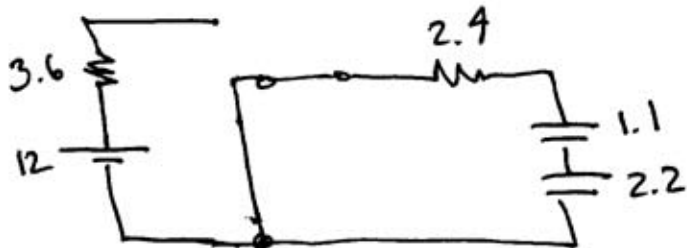


2.



resistors kΩ  
capacitors μF

$$\textcircled{A} \quad V = IR \quad 12 = I(3.6 + 2.4)$$

resistors in series

$$I = 2 \text{ mA}$$

capacitors  
1.1 + 2.2 in series

$$\textcircled{B} \quad Q = VC = (12)(.733) = \underline{\underline{8.80 \mu\text{C}}}$$

③ Capacitors in series same charge

$$V = \frac{Q}{C} = \frac{8.80}{1.1} = \underline{\underline{8 \text{ Volts}}}$$

$$\textcircled{D} \quad Q = Q_s (1 - e^{-t/RC})$$

$$\frac{Q}{Q_s} = .9 = 1 - e^{-t/(6)(.733)}$$

$$.1 = e^{-t/4.4}$$

$$\ln(.1) = -t/4.4$$

$$t = \underline{\underline{10.13 \text{ ms}}}$$

⑤ The time constant for discharging is smaller since it has only one resistor (instead of two in series) (charging to 90% + losing 70% is the equiv so diff is in time constants)