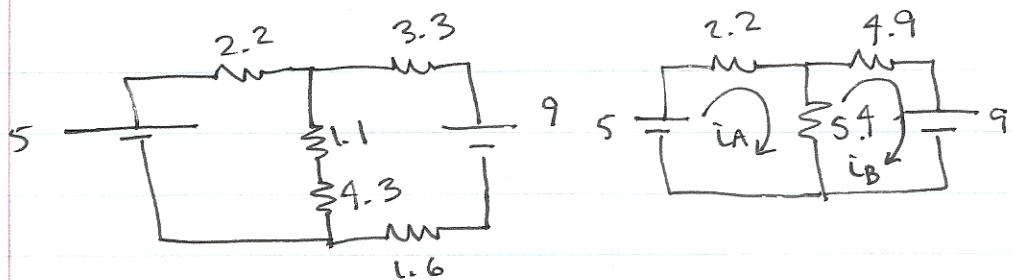


1.1 + 4.3 series
3.3 + 1.6 series



$$\text{Loop A: } 5 = 2.2i_A + 5.4(i_A - i_B)$$

$$-9 = 5.4(i_B - i_A) + 4.9i_B$$

$$5 = 7.6i_A - 5.4i_B$$

$$-9 = -5.4i_A + 10.3i_B$$

$$i_B = -\frac{5}{5.4} + \frac{7.6}{5.4}i_A = -.9259259 + 1.4074074$$

$$-9 = -5.4i_A + 10.3(-.9259259 + 1.4074074)$$

$$-9 = -5.4i_A - 9.53703677 + 14.496296$$

$$.5370 = 9.0962i_A \quad i_B = -.9259 + 1.4074(.0590)$$

$$i_A = .0590 \text{ mA}$$

$$i_B = -.8429 \text{ mA}$$

goes through 2.2 kΩ resistor

goes through 3.3 + 1.6 kΩ resist.

$$i_A - i_B = .0590 - (-.8429) = .9019 \text{ mA}$$

goes through
1.1 + 4.3 kΩ resistors