
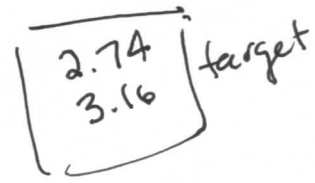


resistors in k Ω

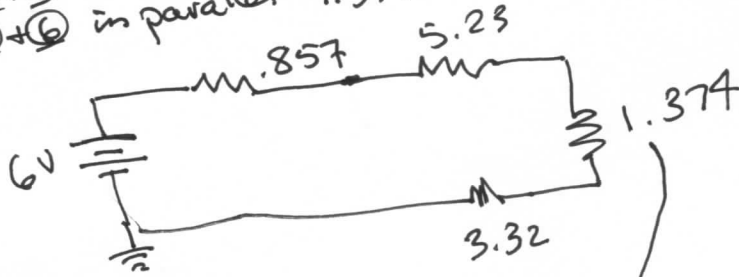

- ①+② in parallel .857
- ③+④ in series 5.23
- ⑤+⑥ in parallel 1.374



all series = 10.781



$$V = IR$$

$$I = \frac{V}{R} = \frac{6}{10.781} = .557$$

This is the current through 2.74k Ω
it is .557 mA

Voltage across $V = IR$
 $(.557)(2.74) = 1.53 \text{ V}$

current through 1.374 is .557
 $V = IR = (.557)(1.374)$
 $= .765 \text{ Volts}$

also is voltage across 3.16k Ω
 $V = IR$ $I = \frac{V}{R} = \frac{.765}{3.16} = .242 \text{ mA}$